

### ③ COMMON COLLECTOR CONFIGURATION (CC)

PAGE: \_\_\_\_\_  
DATE: \_\_\_\_\_

In this configuration input signal is applied between base and collector and output voltage is taken across emitter-collector voltage.

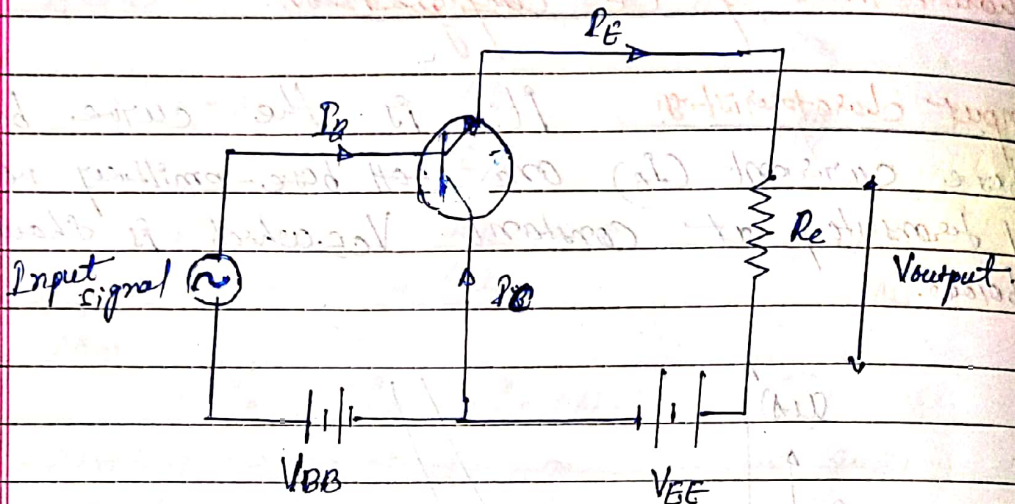


Fig: Common collector configuration

Input  $\alpha$

Current amplification factor ( $\gamma$ ):— It is the ratio of change in emitter current ( $\Delta I_E$ ) to change in base current ( $\Delta I_B$ ). i.e.

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

Relation between  $\gamma$  and  $\alpha$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\alpha \approx \beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\therefore I_E = I_B + I_C$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\text{or } \Delta I_B = \Delta I_E - \Delta I_C$$

putting the value of  $\Delta I_B$  in equation (1) we get:

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

On dividing R.H.S by  $\Delta I_E$  we get:-

$$\gamma = \frac{\frac{\Delta I_E}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{1}{1 - \alpha}$$

$$\gamma = \frac{1}{1 - \alpha}$$

**Input characteristics:-** It is the curve between base current ( $I_B$ ) and base collector voltage at constant emitter collector voltage ( $V_{CE}$ ) is shown below.

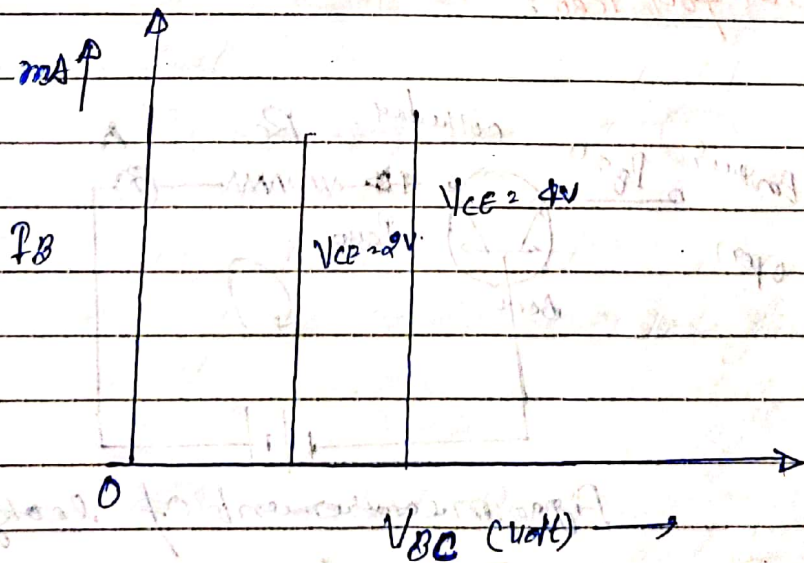


Fig: I/P characteristics of CE configuration

Output characteristics:- It is the curve between emitter current ( $I_E$ ) and emitter-collector voltage ( $V_{EC}$ ) at constant base current ( $I_B$ ) of common emitter.

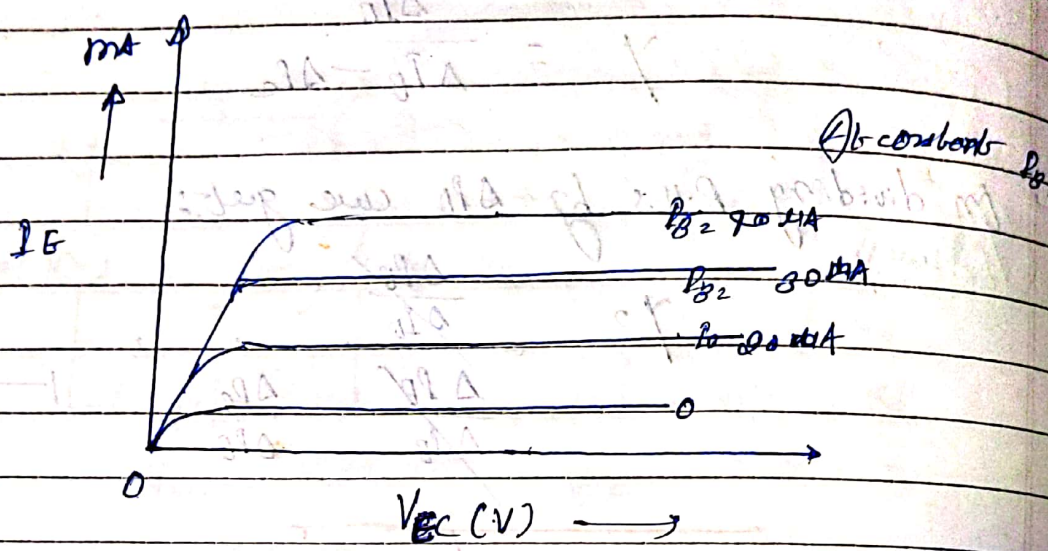


Fig: Output characteristics of CE configuration

Leakage currents in a Transistor.

Leakage current:- It is the reverse current flow through a reverse biased PN junction. The magnitude of leakage current is ~~small~~ very small.

Circuit for  $I_{CBO}$ :

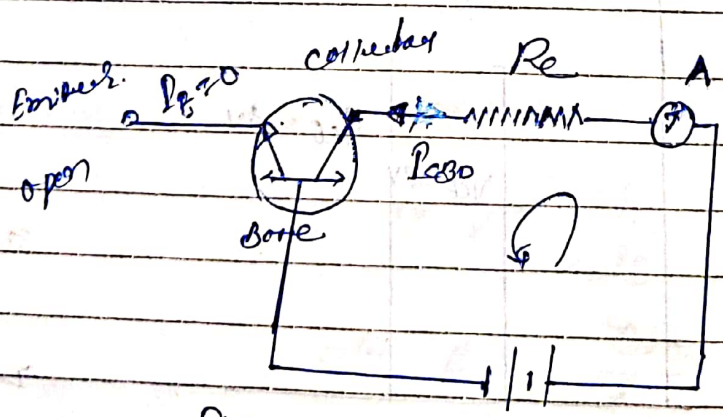


Fig: measurement of leakage current

Ⓢ In a CE circuit,  $I_{CBO}$  is the amount of current that flows in the

collector current due to minority charge carriers shown in fig. when emitter is open.  
It is temperature dependent current for  $I_{CBO}$  it doubles for every  $10^\circ\text{C}$  rise temperature which is 10 to 100 times greater than  $I_{CBO}$   
 $I_{CBO} = 0.01 \mu\text{A}$  to  $1 \mu\text{A}$   
 $I_{CE} = 0$  to  $15 \mu\text{A}$

Circuit for  $I_{CBO}$

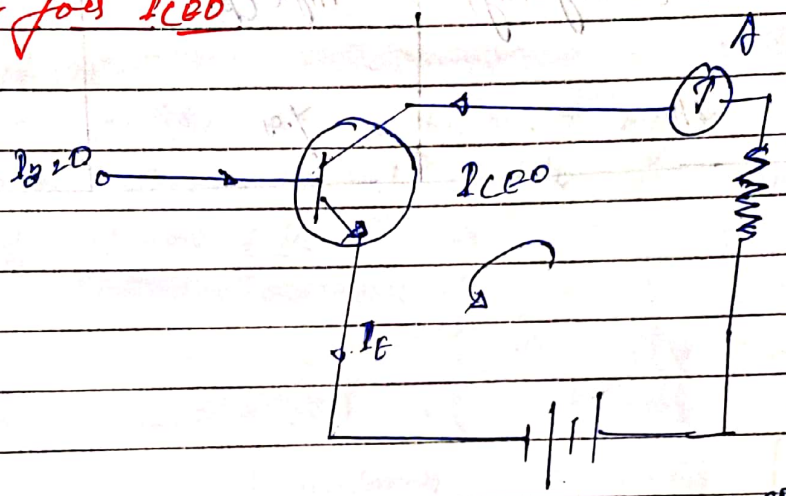


Fig. Measurement of leakage current in CE circuit.

Expression for collector/emitter currents for CC mode operation:

we know that

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (I)}$$

$$\text{Also } I_E = I_B + I_C \quad \text{--- (II)}$$

putting the value of  $I_C$  in equation (I) we get:

$$\therefore I_E = I_B + I_C \quad \left\{ \begin{array}{l} I_E = \frac{1}{(1-\alpha)} I_B + \frac{I_{CBO}}{(1-\alpha)} \\ \therefore I_C = I_E \end{array} \right.$$

$$I_E = I_B + \alpha I_E + I_{CBO} \quad \therefore I_C = I_E$$

$$I_E - \alpha I_E = I_B + I_{CBO}$$

$$I_E(1-\alpha) = I_B + I_{CBO}$$

$$\therefore I_C = \frac{1}{(1-\alpha)} I_B + \frac{I_{CBO}}{(1-\alpha)}$$

$$I_C = (\beta+1) I_B + \beta I_{CBO}$$

# Performance Comparison among the configurations (cases)

DATE: / /

Characteristics	Common Base (CB)	Common emitter (CE)	Common collector (CC)
i) Input Impedance	Lowest	moderate	Highest
ii) Output impedance	Highest	moderate	Lowest
iii) Voltage gain	High	very high	nearly unity
iv) Current gain	1 (nearly unity)	High ( $\beta$ )	Highest ( $\beta+1$ )
v) phase reversal	No	Yes	No.