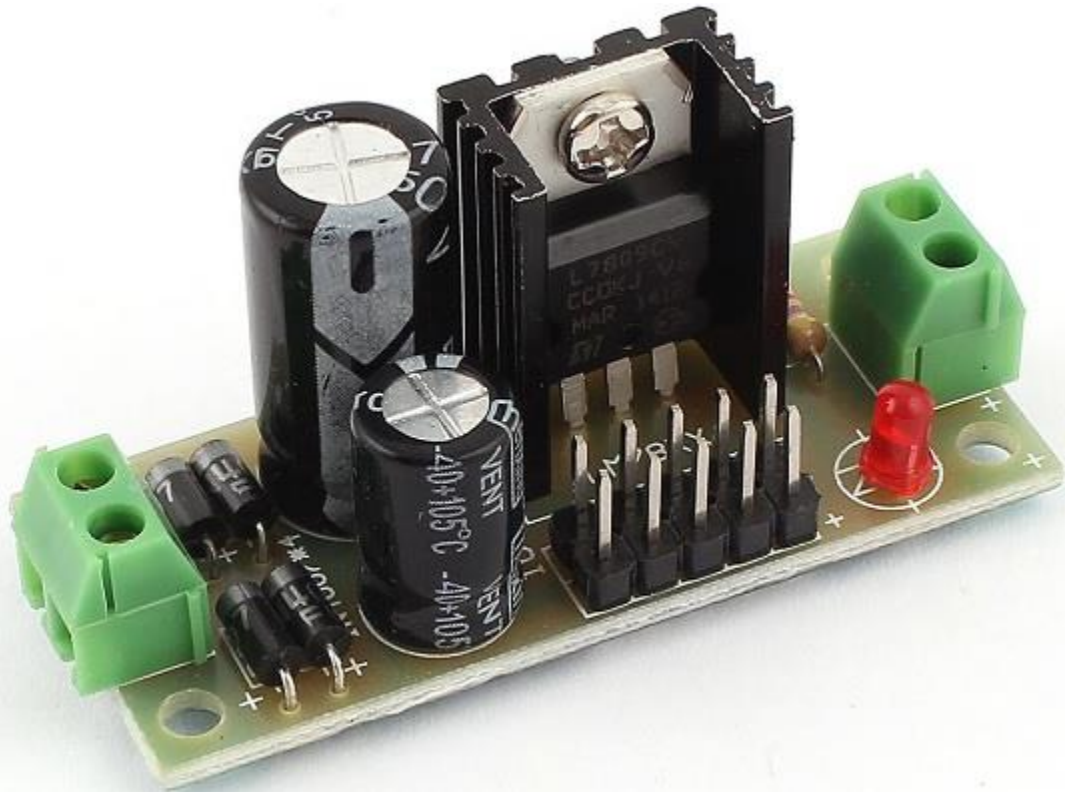

The part of electronics that deal with the control and conversion of electric power can be termed as **Power Electronics**. A regulator is an important device when it comes to power electronics as it controls the power output.

Need for a Regulator

For a Power supply to produce a constant output voltage, irrespective of the input voltage variations or the load current variations, there is a need for a voltage regulator.

A **voltage regulator** is such a device that maintains constant output voltage, instead of any kind of fluctuations in the input voltage being applied or any variations in current, drawn by the load. The following image gives an idea of what a practical regulator looks like.



Types of Regulators

Regulators can be classified into different categories, depending upon their working and type of connection.


Depending upon the type of regulation, the regulators are mainly divided into two types namely, line and load regulators.

- **Line Regulator** – The regulator which regulates the output voltage to be constant, in spite of input line variations, it is called as **Line regulator**.
- **Load Regulator** – The regulator which regulates the output voltage to be constant, in spite of the variations in load at the output, it is called as **Load regulator**.

Depending upon the type of connection, there are two type of voltage regulators. They are

- Series voltage regulator
- Shunt voltage regulator

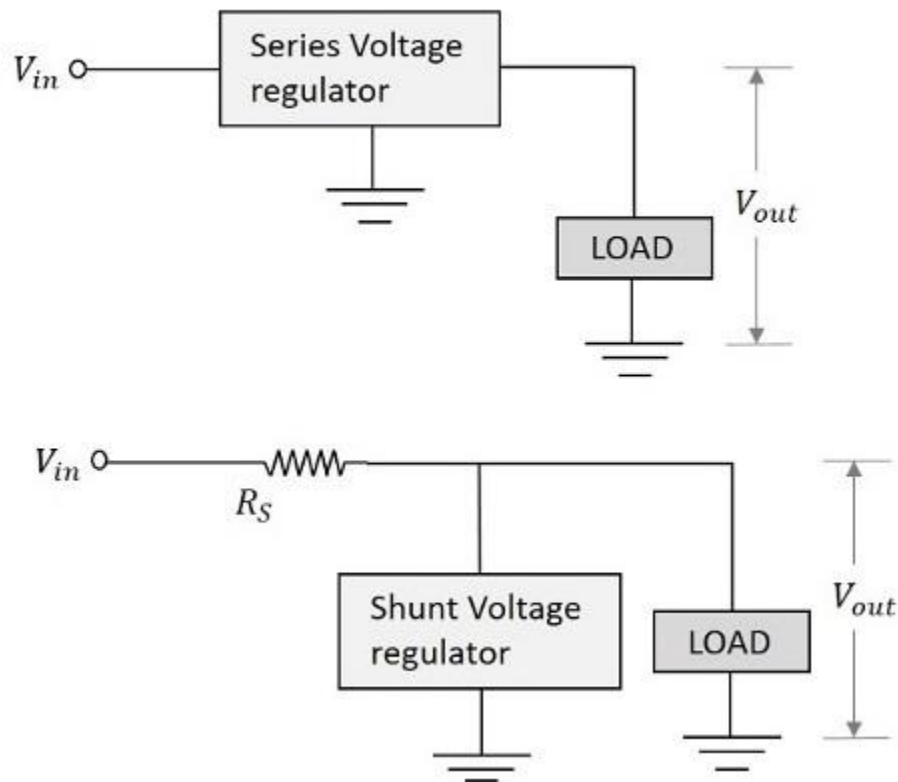The arrangement of them in a circuit will be just as in the following figures.




Let us have a look at other important regulator types.

Zener Voltage Regulator

A Zener voltage regulator is one which uses Zener diode for regulating the output voltage. We have already discussed the details regarding Zener diode in BASIC ELECTRONICS tutorial.

When the Zener diode is operated in the breakdown or **Zener region**, the voltage across it is substantially **constant** for a **large change of current** through it. This characteristic makes Zener diode a **good voltage regulator**.

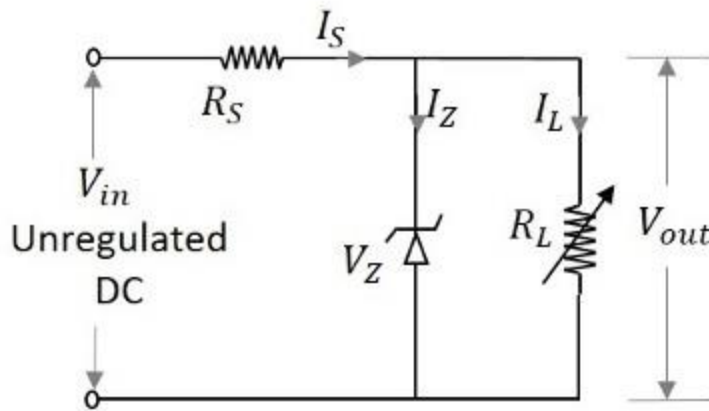The following figure shows an image of a simple Zener regulator.



The applied input voltage V_i when increased beyond the Zener voltage V_Z , then the Zener diode operates in the breakdown region and maintains constant voltage across the load. The series limiting resistor R_S limits the input current.

Working of Zener Voltage Regulator

The Zener diode maintains the voltage across it constant in spite of load variations and input voltage fluctuations. Hence we can consider 4 cases to understand the working of a Zener voltage regulator.

Case 1 – If the load current I_L increases, then the current through the Zener diode I_Z decreases in order to maintain the current through the series resistor R_S constant. The output voltage V_o depends upon the input voltage V_i and voltage across the series resistor R_S .

This is can be written as

$$V_o = V_{in} - I R_S$$

Where I is constant. Therefore, V_o also remains constant.

Case 2 – If the load current I_L decreases, then the current through the Zener diode I_Z increases, as the current I_S through R_S series resistor remains constant. Though the current I_Z through Zener diode increases it maintains a constant output voltage V_Z , which maintains the load voltage constant.

Case 3 – If the input voltage V_i increases, then the current I_S through the series resistor R_S increases. This increases the voltage drop across the resistor, i.e. V_{S} increases. Though the current through Zener diode I_Z increases with this, the voltage across Zener diode V_Z remains constant, keeping the output load voltage constant.

Case 4 – If the input voltage decreases, the current through the series resistor decreases which makes the current through Zener diode I_Z decreases. But the Zener diode maintains output voltage constant due to its property.

Limitations of Zener Voltage Regulator


There are a few limitations for a Zener voltage regulator. They are –

- It is less efficient for heavy load currents.
- The Zener impedance slightly affects the output voltage.

Hence a Zener voltage regulator is considered effective for low voltage applications. Now, let us go through the other types of voltage regulators, which are made using transistors.

Transistor Series Voltage Regulator

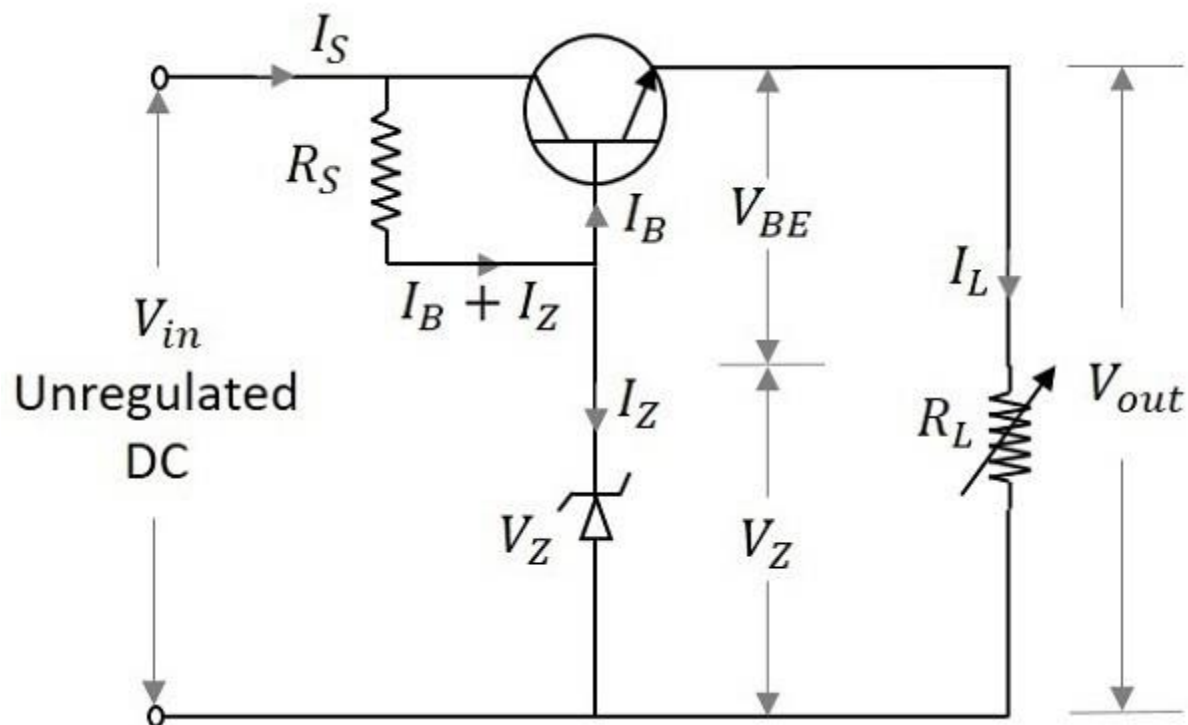This regulator has a transistor in series to the Zener regulator and both in parallel to the load. The transistor works as a variable resistor regulating its collector emitter voltage in order to maintain the output voltage constant. The figure below shows the transistor series voltage regulator.



With the input operating conditions, the current through the base of the transistor changes. This effects the voltage across the base emitter junction of the transistor V_{BE} . The output voltage is maintained by the Zener voltage V_Z which is constant. As both of them are maintained equal, any change in the input supply is indicated by the change in emitter base voltage V_{BE} .

Hence the output voltage V_o can be understood as

$$V_o = V_Z + V_{BE}$$

Working of Transistor Series Voltage Regulator

The working of a series voltage regulator shall be considered for input and load variations. If the input voltage is increased, the output voltage also increases. But this in turn makes the voltage across the

collector base junction V_{BE} to decrease, as the Zener voltage V_Z remains constant. The conduction decreases as the resistance across emitter collector region increases. This further increases the voltage across collector emitter junction V_{CE} thus reducing the output voltage V_O . This will be similar when the input voltage decreases.

When the load changes occur, which means if the resistance of the load decreases, increasing the load current I_L , the output voltage V_O decreases, increasing the emitter base voltage V_{BE} .

With the increase in the emitter base voltage V_{BE} the conduction increases reducing the emitter collector resistance. This in turn increases the input current which compensates the decrease in the load resistance. This will be similar when the load current increases.

Limitations of Transistor Series Voltage Regulator


Transistor Series Voltage Regulators have the following limitations –

- The voltages V_{BE} and V_Z are affected by the rise in temperature.
- No good regulation for high currents is possible.
- Power dissipation is high.
- Power dissipation is high.
- Less efficient.

To minimize these limitations, transistor shunt regulator is used.

Transistor Shunt Voltage Regulator

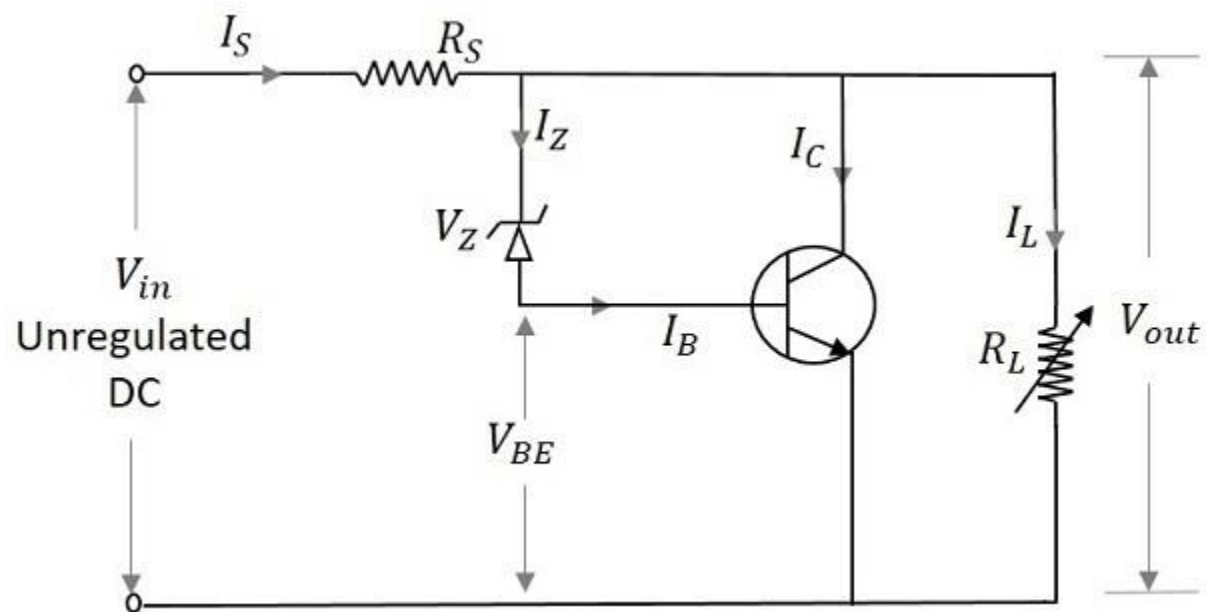A transistor shunt regulator circuit is formed by connecting a resistor in series with the input and a transistor whose base and collector are connected by a Zener diode that regulates, both in parallel with the load. The figure below shows the circuit diagram of a transistor shunt regulator.



Working of Transistor Shunt Voltage Regulator

If the input voltage increases, the V_{BE} and V_{O} also gets increased. But this happens initially. Actually when V_{in} increases, the current I_{in} also increases. This current when flows through R_S , causes a voltage drop V_S across the series resistor, which also gets increased with V_{in} . But this makes V_{O} to decrease. Now this decrease in V_{O} compensates the initial increase maintaining it to be constant. Hence V_{O} is maintained constant. If the output voltage decreases instead, the reverse happens.

If the load resistance decreases, there should be decrease in the output voltage V_{O} . The current through the load increases. This makes the base current and collector current of the transistor to decrease. The voltage across the series resistor becomes low, as the current flows heavily. The input current will be constant.

The output voltage appears will be the difference between the applied voltage V_i and the series voltage drop V_S . Hence the output voltage will be increased to compensate the initial decrease and hence maintained constant. The reverse happens if the load resistance increases.

IC Regulators

Voltage Regulators are now-a-days available in the form of Integrated Circuits (ICs). These are in short called as IC Regulators.

Along with the functionality like a normal regulator, an IC regulator has the properties like thermal compensation, short circuit protection and surge protection which are built into the device.

Types of IC regulators

IC regulators can be of the following types –


- Fixed Positive voltage regulators
- Fixed Negative voltage regulators
- Adjustable voltage regulators
- Dual-tracking voltage regulators

Let us now discuss them in detail.

Fixed Positive Voltage Regulator

The output of these regulators is fixed to a specific value and the values are positive, which means the output voltage provided is positive voltage.

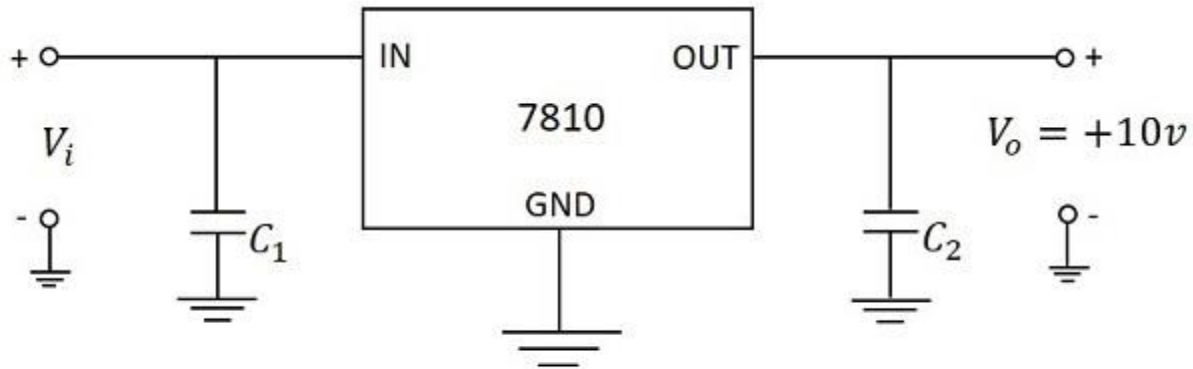The most used series is 7800 series and the ICs will be like IC 7806, IC 7812 and IC 7815 etc. which provide +6v, +12v and +15v respectively as output voltages. The figure below shows the IC 7810 connected to provide a fixed 10v positive regulated output voltage.




Fixed Positive Voltage Regulator

In the above figure, the input capacitor C_1 is used to prevent unwanted oscillations and the output capacitor C_2 acts as a line filter to improve transient response.

Fixed Negative Voltage Regulator

The output of these regulators is fixed to a specific value and the values are negative, which means the output voltage provided is negative voltage.

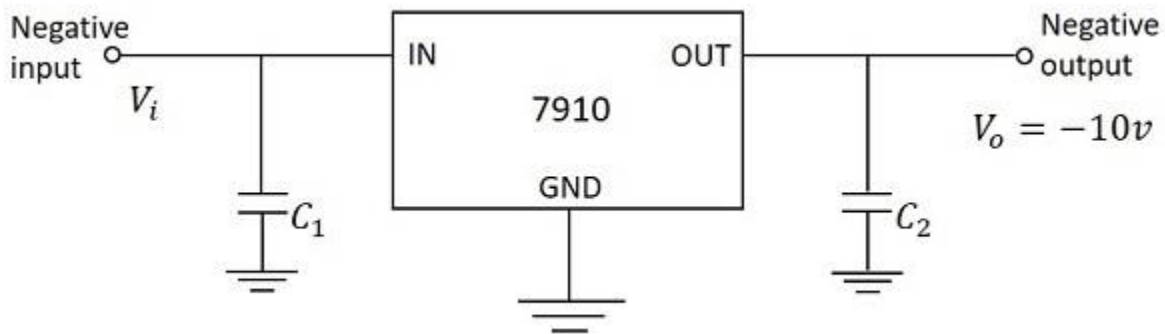
The most used series is 7900 series and the ICs will be like IC 7906, IC 7912 and IC 7915 etc. which provide -6v, -12v and -15v respectively as output voltages. The figure below shows the IC 7910 connected to provide a fixed 10v negative regulated output voltage.



In the above figure, the input capacitor C_1 is used to prevent unwanted oscillations and the output capacitor C_2 acts as a line filter to improve transient response.

Adjustable Voltage Regulators

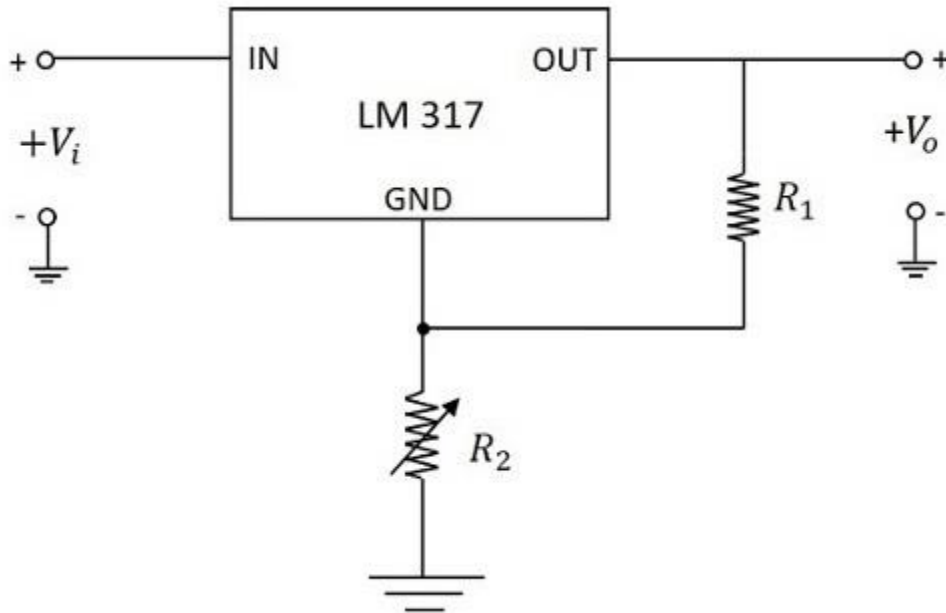
An adjustable voltage regulator has three terminals IN, OUT and ADJ. The input and output terminals are common whereas the adjustable terminal is provided with a variable resistor which lets the output to vary between a wide range.



The above figure shows an unregulated power supply driving a LM 317 adjustable IC regulator which is commonly used. The LM 317 is a three terminal positive adjustable voltage regulator and can supply 1.5A of load current over an adjustable output range of 1.25v to 37v.

Dual-Tracking Voltage Regulators

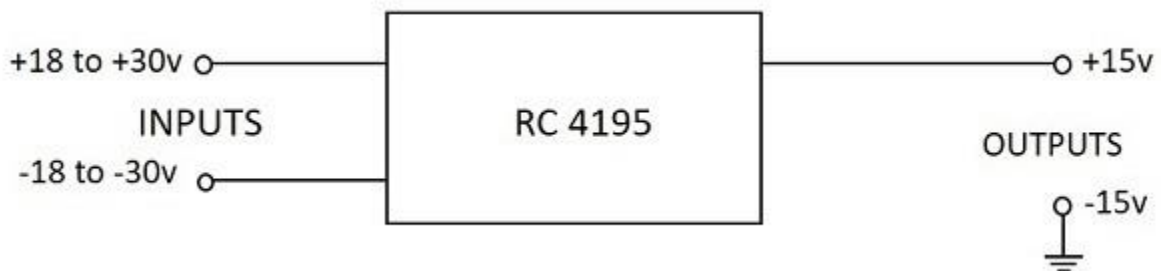A dual-tracking regulator is used when split-supply voltages are needed. These provide equal positive and negative output voltages. For example, the RC4195 IC provides D.C. outputs of +15v and -15v. This needs two unregulated input voltages such as the positive input may vary from +18v to +30v and negative input may vary from -18v to -30v.



The above image shows a dual-tracking RC4195 IC regulator. The adjustable dual-tracking regulators are also available whose outputs vary between two rated limits.



