



∴ The armature current  $I_a$  is given by

$$I_a = \frac{E - E_b}{R_a} \quad \text{--- (1)}$$

At starting speed  $\omega = 0$ .

$$\Rightarrow E_b = 0.$$

$$\text{So, } I_a = \frac{E}{R_a}$$

Since, the armature winding electrical resist.  $R_a$  is ~~very~~ very small, this motor has a ~~very~~ high starting current in absence of back emf or a circuit we ~~need~~ need a starter to start the motor.

### Types of DC motors

There are five types of DC motors.

- i) permanent magnet DC motor
- ii) Separately excited DC motor
- iii) Series wound DC motor
- iv) Shunt wound DC motor
- v) Compound wound DC motor.

### permanent magnet DC motor

It consists of an armature and one or several permanent magnet encircling the armature. Field coils are usually not required. However some of these motor do have coils wound on the poles. If they exist, these coils are intended only for recharging the magnets in the event that they loose.





strength.

ii) Separately - Excited DC motor. These motor have field coils similar to those of a shunt wound machine, but the armature and field coils are fed from different sources as shown below.

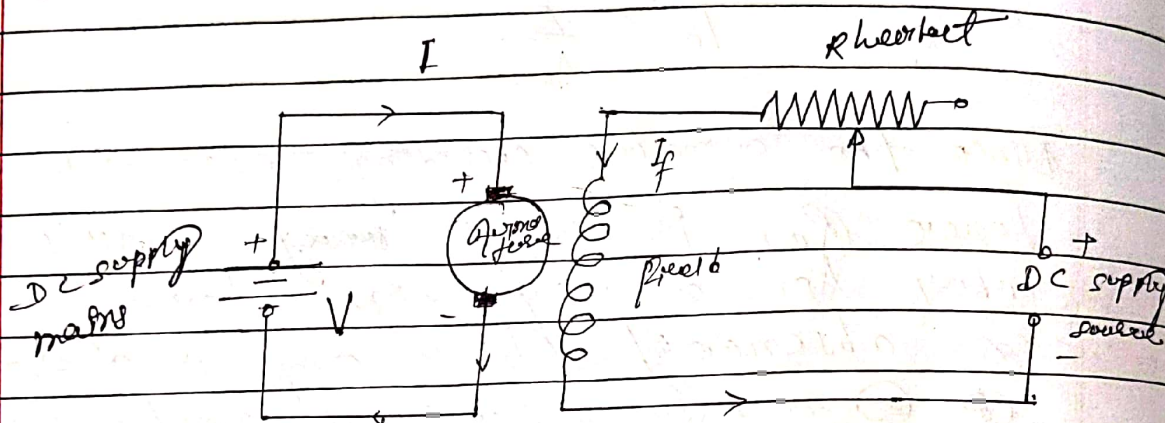


Fig: Separately - Excited DC motor

Let

Armature current,  $I_a =$  Line current

$I_f = I$  (say)

Back emf developed,  $E_b = V - I R_a$

where

$R_a =$  Resistance of armature

So, power drawn from supply,

$$P = IV$$

So, Mechanical power developed,  $P_m =$  D/P power

power

lost in armature

$$= VI - I^2 R_a$$


$$= I(V - I R_a)$$

$$[ P_m = I E_b ]$$


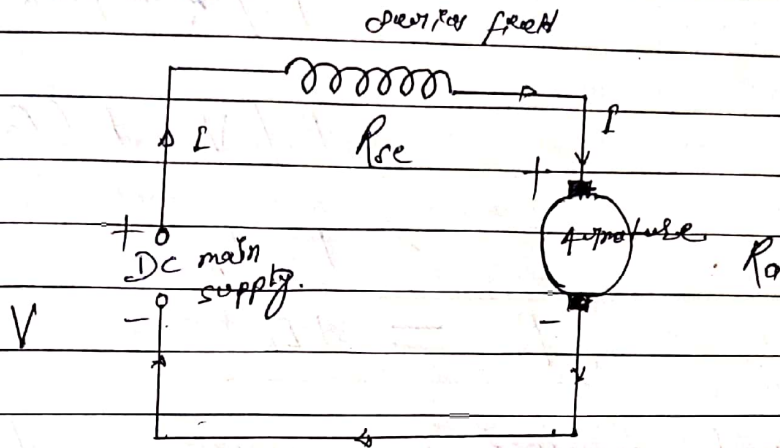
### III) Series wound DC motor.

In this DC motor, the field coils, consists of few turns of thick wire, are connected in series with the armature as shown below



figs Series wound DC motor.

The cross-sectional area of the wire used for field coil are large to carry the armature current, but owing to heavy current the no. of turns of wire need not be large.

From figure, we have,

Let, Armature current  $I_a =$  series field current  $I_{se}$

$\therefore$  Line current  $I_L = I$

$\therefore$  Back emf developed by the coil,

$$E_b = V - I(R_a + R_{se}) \quad \text{--- (1)}$$

So,

The power drawn from source  $P = IV$ .

$\therefore$  The mechanical power delivered  $= I \cdot P$  power - power dissipated in armature and field



Date \_\_\_/\_\_\_/\_\_\_



$$P_m = IV - I^2(R_o + R_{se})$$

$$= I [V - I(R_o + R_{so})]$$

$$= I [V - I(R_o + R_{so})]$$

$$= I [V - I(R_o + R_{se})]$$

$$= I \cdot E_b$$

$$P_m = I E_b$$