

Principle of chopper operation.

Principle of a chopper is a high speed ON/OFF semiconductor switch. It connects source to load and disconnects the load from source at fast speed. By doing this, a chopped load voltage is obtained from a constant DC supply of magnitude V_s . The below figure shows the basic circuit for the operation of chopper.

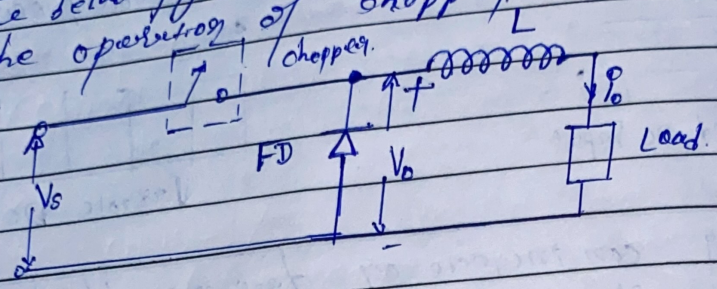


Fig: Chopper circuit.

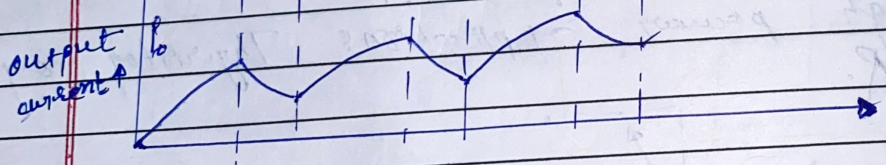
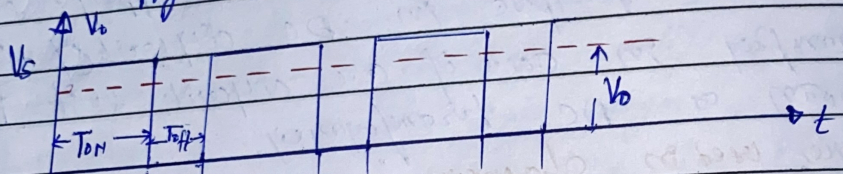


Fig: Output voltage and current waveform.

Here for the sake of highlighting the principle of chopper operation, the capacitor used for controlling the on, off period of the switch is not shown.

During the period T_{on} , the chopper is ON and the load voltage is equal to source voltage V_s . During the interval T_{off} chopper is OFF

The load current flows through the free-wheeling diode FD as a result of this load terminals are short circuited by FD and load voltage is 0. In this manner, a chopped dc voltage is produced at the load terminals.

The load current varies as shown in figure where during T_{on} , the load current rises whereas during T_{off} , the load current decays.

So, The average load voltage is given by

$$V_o = \frac{T_{on}}{T_{on} + T_{off}} \times V_s$$

$$V_o = \frac{T_{on}}{T} V_s$$

where
 T_{on} = ON time
 T_{off} = off time
 T = time period.

$$\frac{T_{on}}{T} = d \text{ (duty cycle)}$$

$$V_o = d V_s$$

$$V_o = T_{on} f V_s$$

$$f = \frac{1}{T}$$

So, by changing the value of d we can change the load voltage.

Control strategies

The operation of chopper is controlled by



Fig

- Time Ratio Control (TRC)
- Current limit control.

Time Ratio control (TRC) In this scheme the on-time ratio T_{on}/T is varied. In this method strategy two methods are used. strategies are

- Constant frequency system.
- Variable frequency system.
- Constant frequency system.

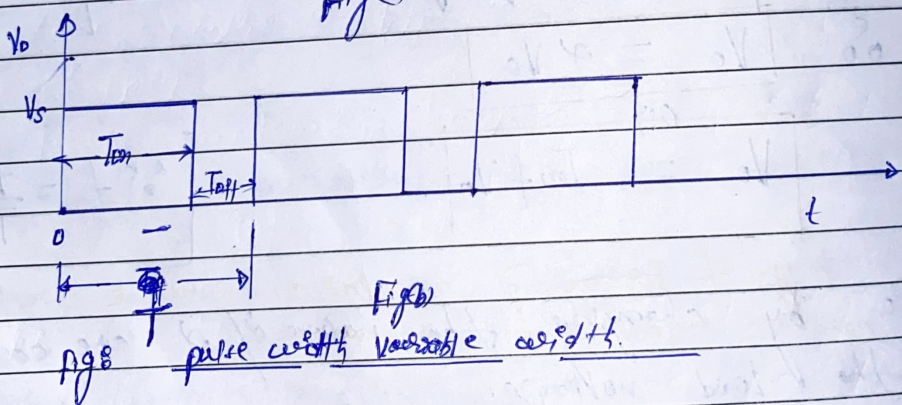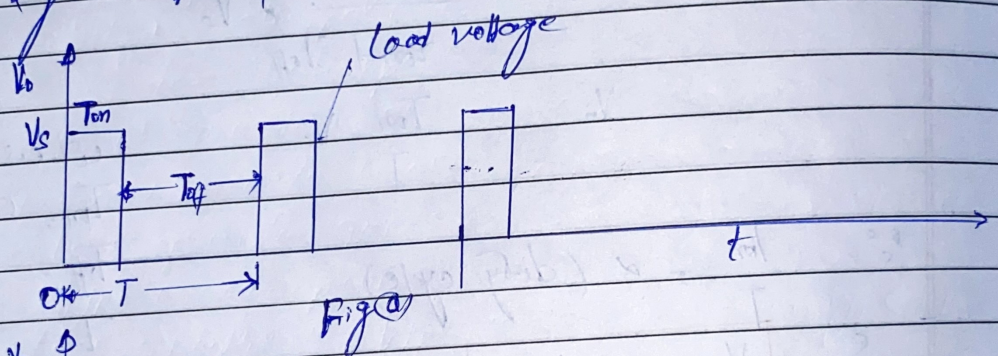In this scheme the ON time is varied but chopping frequency (f) remains the same. This is achieved by PWM technique schemes shown below!



In fig (a) $\alpha = 0.25$

Then $T_{on} = \frac{1}{4} T$

In fig (b) $\alpha = 0.75$

$\therefore T_{on} = \frac{3}{4} T$

Ideally a com varies from 0 to unity. Therefore outp. voltage can vary from 0 to V_c .

Variable Frequency system: In this technique (scheme) variable chopping frequency f is varied and either T_{on} is kept constant or T_{off} time is kept constant. This scheme is shown below.

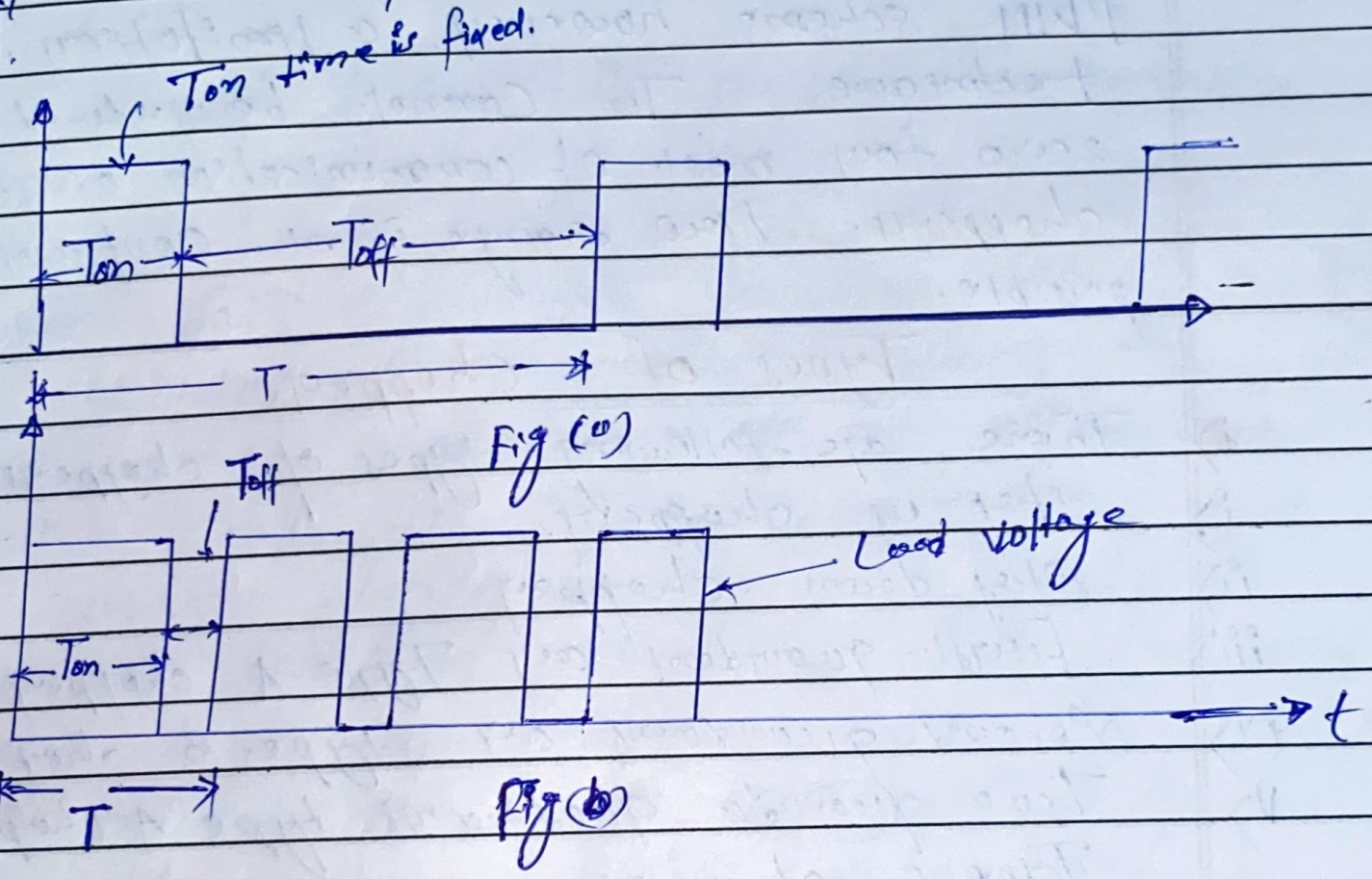


Fig: Variable frequency system waveform.

In the above figures the ON time (T_{on}) is kept fixed while T_{off} is varied and hence α changes.