

# Registers

Registers - A register is a collection of flip-flop. A flip-flop is used to store single bit digital data. To store a large no. of bits the storage capacity is increased by grouping more than one flip-flop. e.g. If we want to store an  $n$ -bit word, we have to use  $n$ -bit registers containing  $n$ -no. of flip flop.

The binary data in a register can be moved within the register from one flip-flop to another. The registers that allow such data transfers are called as shift registers. Types of shift registers -

- i) Serial input serial output (SISO)
- ii) Serial input parallel output (SIPO)
- iii) parallel input serial output (PISO)
- iv) parallel input parallel output (PIPO).

Serial input serial output (SISO) register: The register in which the data is entered in serially and taken out serially is called serial in serial out register (SISO).


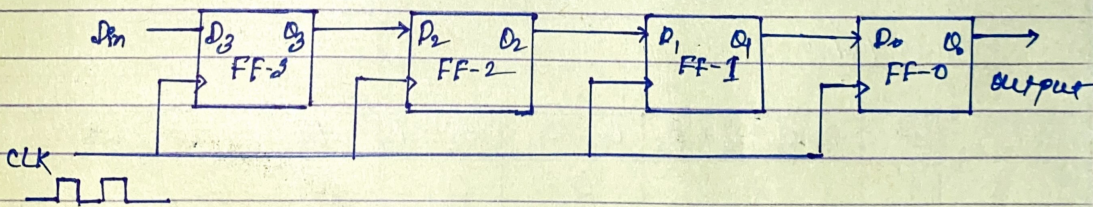


Fig: Block diagram of SISO.

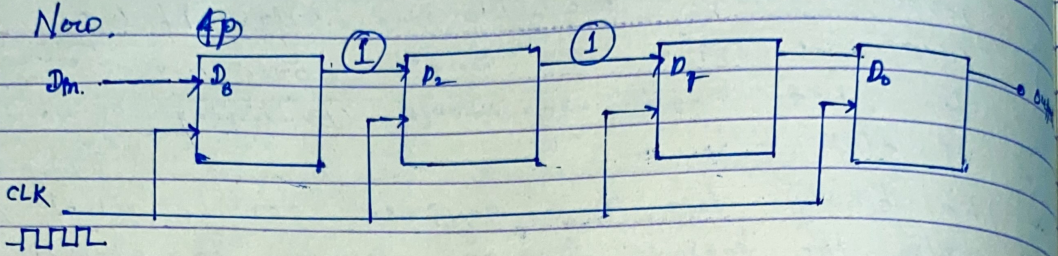
## operations

Let all the flip-flop be initially in the reset condition i.e.  $Q_3 = Q_2 = Q_1 = Q_0 = 0$ . If an input data 1111 applied to the  $D_{in}$  of register. So,  $D_{in} = 1, 1, 1, 1$ . Now apply the clock. On the first falling edge of clock the FF-3 is set and the stored word in the register is  $1000 = Q_3 Q_2 Q_1 Q_0$

Apply the next bit to  $D_3 = 1$ . As soon as the next negative edge of clock hits, FF-2 will set and the stored word is changed to  $Q_3 Q_2 Q_1 Q_0 = 1100$ .



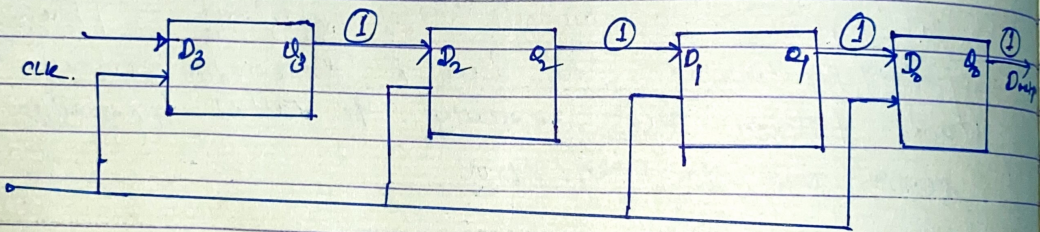Now, Apply the next bit to be stored i.e. 1. Apply the next clock pulse. As soon as the third negative clock edge hits, FF-1 will be set and output to be modified to  $Q_3 Q_2 Q_1 Q_0 = 1110$ . Similarly, with  $D_3 = 1$  on fourth falling edge of -ve clock edge, the output gets modified.



Truth table:

CLK	$D_3 = Q_3$	$D_2 = Q_3$	$Q_2 = D_1$	$Q_1 = D_0$	$Q_0$
		0	0	0	0
↓	1 →	1	0	0	0
↓	1 →	1 →	1	0	0
↓	1 →	1 →	1 →	1	0
↓	1 →	1 →	1 →	1 →	1

Fig: Direction of data travel

Waveform

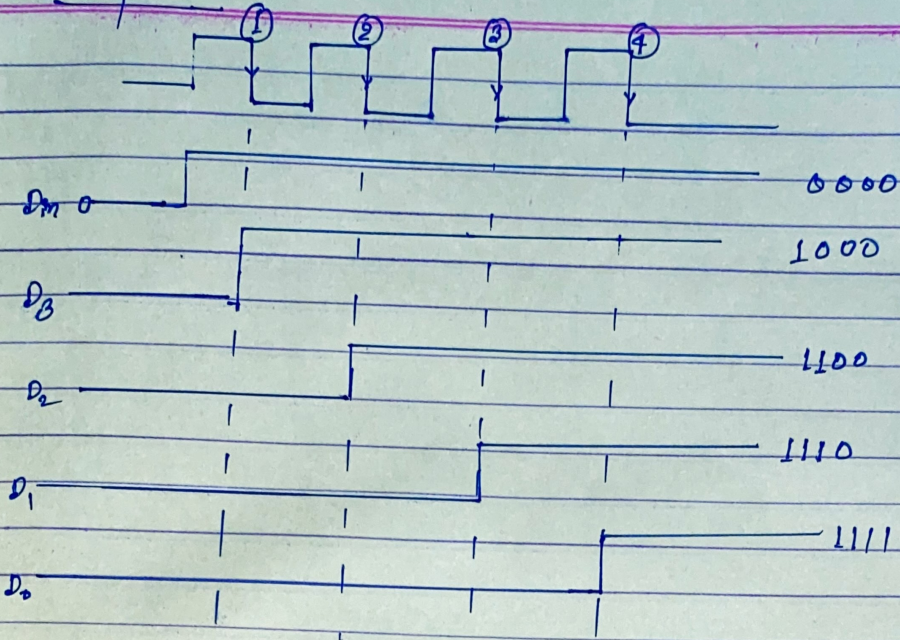


Fig: Operational waveform of SISO.