

DR.SHYAMA PRASAD MUKHERJEE UNIVERSITY, RANCHI

UNIVERSITY DEPARTMENT OF ELECTRONICS

Subject : Electronics Semester- 3rd Paper : cc –v

GROUP ~ (A)

Multiple choice Question

- (1) The voltage gain of a transistor connected in.....arrangement the highest.
a. Common base b. common collector c. common emitter d. none of these
- (2) The operating point is also called the.....
a. cutoff point b. quiescent point c. saturation point d. none of these
- (3) The maximum efficiency of a half wave rectifier is.....
a. 40.6 % b. 81.8 % c. 50 % d. 25 %
- (4) The most widely used rectifier is.....
a. Half wave rectifier b. center tap full wave rectifier
b. Bridge full wave rectifier d. none of the above
- (5) Emitter following is also known as---
a. Grounded emitter circuit c. grounded base circuit
b. Grounded collector circuit d. none of the above
- (6) The PIV rating of each diode in bridge rectifier is.....that of the equivalent Centre tap rectifier.
a. One half b. the same as c. twice d. four times
- (7) A transistor is aoperated device.
a. Current b. voltage c. both a & b d. none of the above
- (8) A Zener diode is used as-
a. An amplifier b. a voltage regulator c. a rectifier d. a multivibrator
- (9) The leakage current in a crystal diode is due to.....
a. Minority carriers b. majority carriers c. junction capacitance d. none of the above
- (10) The emitter of a transistor isdoped.
a. Lightly b. heavily c. moderately d. none
- (11) A Pn junction acts as a.....
a. Controlled switch b. bidirectional switch c. unidirectional switch d, none of the above
- (12) The relation between β and α is
- a. $\beta = \frac{1}{1-\alpha}$ b. $\beta = \frac{1-\alpha}{\alpha}$ c. $\beta = \frac{\alpha}{1-\alpha}$ d. $\beta = \frac{\alpha}{1+\alpha}$
- (13) The most commonly used transistor arrangement isarrangement
a. Common emitter b. common base c. common collector d. none

- (14) When negative voltage feedback is applied to an amplifier, its voltage gain.....
 a. Is increased b. is reduced c. remains the same d. none
- (15) The voltage of negative feedback fraction is always
 a. Less than 1 b. more than 1 c. equal to 1 d. none
- (16) The input impedance of a transistor connected inarrangement is the highest
 a. Common emitter b. common collector c. common base d. none of these
- (17) The basic purpose of applying negative voltage feedback is to
 a. Increase voltage gain b. reduce distortion
 c. keep the temperature within limits d. none of the above
- (18) The ripple factor of a half -wave rectifier is
 a. 1.21 b. 2.5 c. 2 d. 0.48
- (19) when a pentavalent impurity is added to a pure semiconductor, it becomes.....
 a. an insulator b. an intrinsic semiconductor c. p-type semi-conductor d. n-type semi-conductor
- (20) In the depletion region of a PN junction, There is a shortage of
 a. acceptor ions b. holes and electrons c. donor ions d. none of the above

GROUP- B

Short answer type question

- (1) What is ideal diode ? what its advantage and disadvantages .
- (2) What is rectifier ? Explain half wave rectifier with its circuit diagram.
- (3) What is transistor ? Explain its type with symbol.
- (4) What is negative feedback? Explain it with diagram.
- (5) Show the relation between α and β function .
- (6) Write the advantage of negative voltage feedback.
- (7) Explain barkhausen criterion.
- (8) Compare the various characteristics of the three connection configuration.
- (9) What is Q-point transistor? Also draw its graph.
- (10) What is DC load line in a transistor ?

GROUP -C

Long answer type question.

- (1) Explain the full wave rectifier with diagram , working and waveforms and find its D.C current and voltage ,ripple factor and efficiency.
- (2) Explain and draw the common emitter configuration of transistor and its input and output characteristics graph.
- (3) Draw and explain the circuit diagram of Hartley oscillator.
- (4) Explain the working PNP transistor in common base (CB) connection. Also draw its input and output characteristics.
- (5) Draw and explain how transistor works as an amplifier.
- (6) Explain the full wave rectifier with diagram ,working and wave forms also find the d.c current and voltage ,ripple factor &efficiency.